

- **Name:** Jheboy B. Asid
- **Term:** 2nd

Laboratory Experiment 002: Operational Amplifiers

This Jupyter Notebook demonstrates different operational amplifier (Op-Amp) configurations with Python simulations.

Configurations Covered:

1. Inverting Amplifier
2. Non-Inverting Amplifier
3. Voltage Follower (Buffer)
4. Summing Amplifier
5. Integrator
6. Differentiator


Each section contains code to simulate the respective amplifier behavior and plots the output waveform.

```
In [1]: import numpy as np
import matplotlib.pyplot as plt
import scipy.signal as signal

# Time vector for simulation
t = np.linspace(0, 1, 1000)
Vin = np.sin(2 * np.pi * 5 * t) # Input signal (5 Hz sine wave)

# Define common parameters
Rf, Rin, R1, R2, C = 10e3, 1e3, 1e3, 1e3, 1e-6

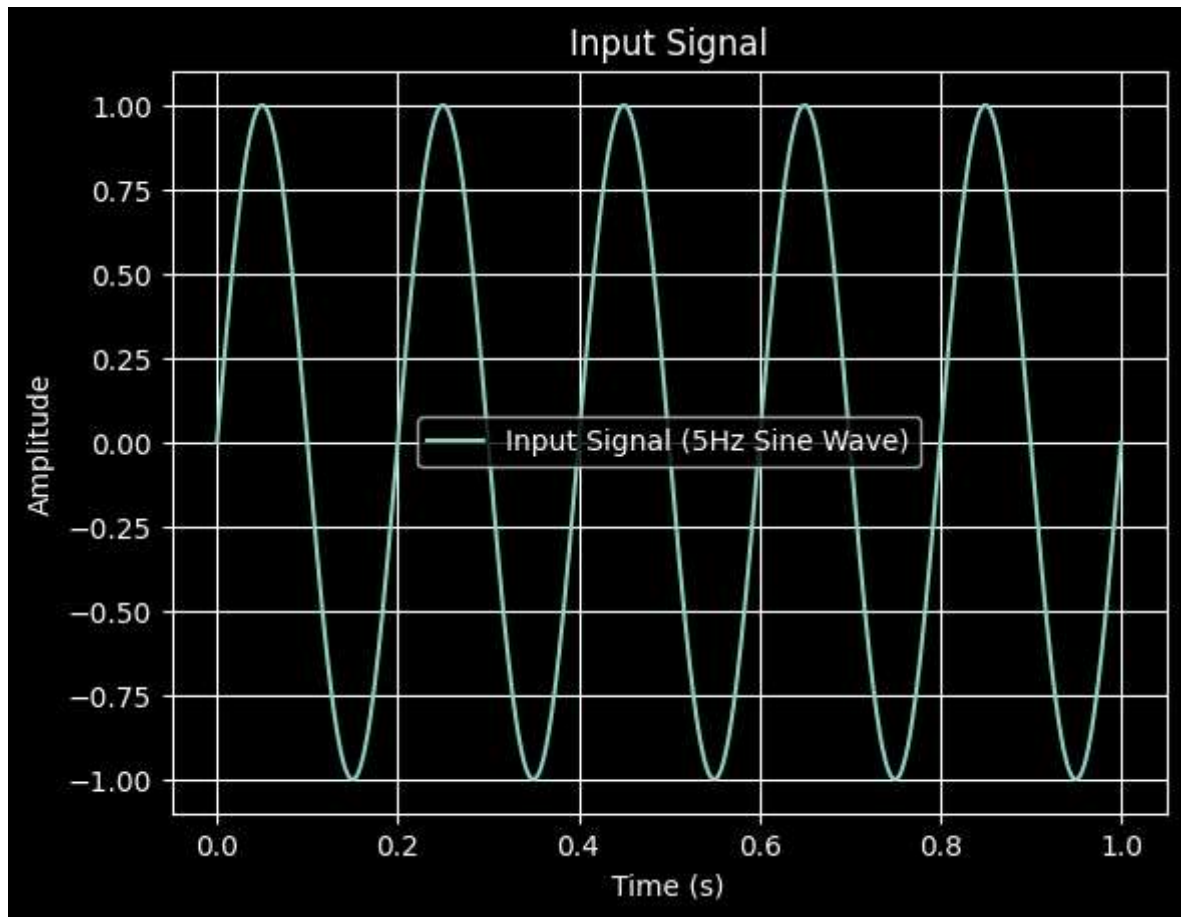
# Plot Input Signal
plt.figure()
plt.plot(t, Vin, label='Input Signal (5Hz Sine Wave)')
plt.title('Input Signal')
plt.xlabel('Time (s)')
plt.ylabel('Amplitude')
plt.grid('true')
plt.legend()
plt.show()
```



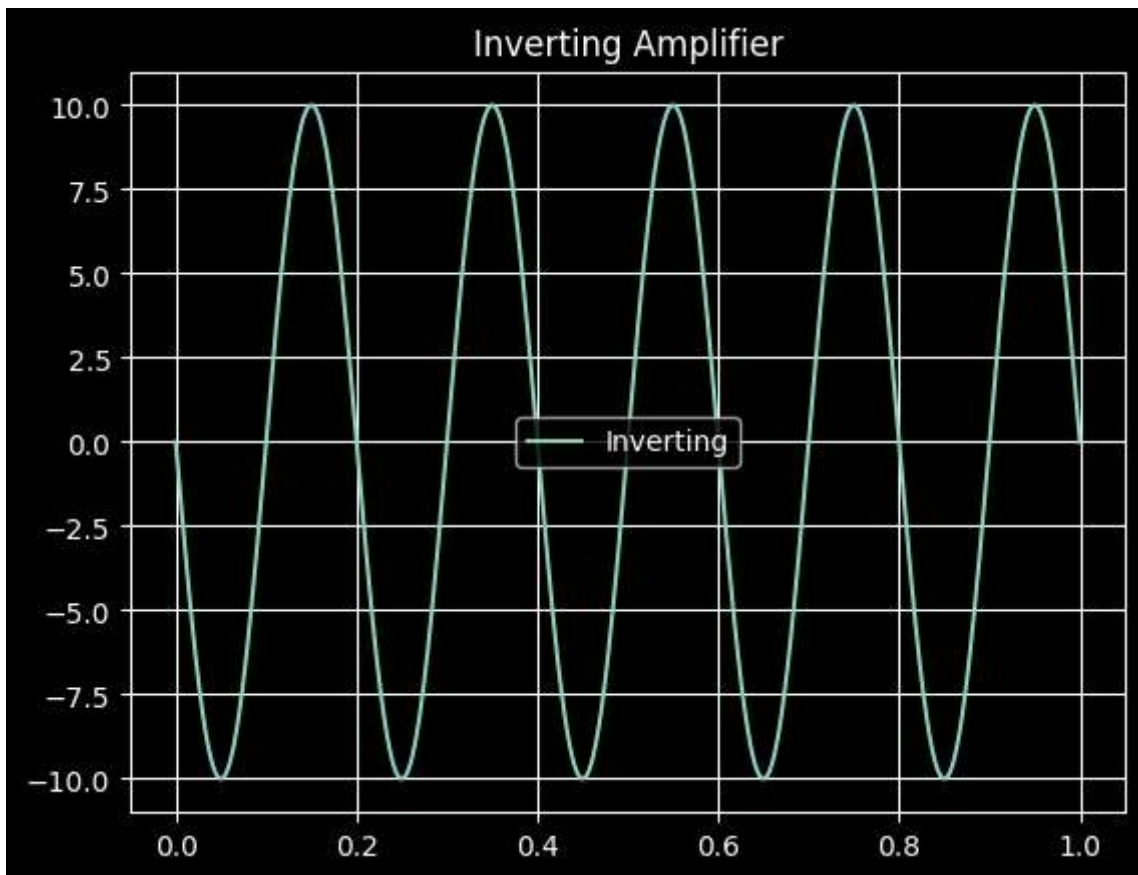1. Inverting Amplifier

$$V_o = -(R_f/R_i) * V_i$$

```
In [3]: def inverting_amplifier(Vin, Rf, Rin):  
        Av = -Rf / Rin  
        return Av * Vin  
  
Vout_inv = inverting_amplifier(Vin, Rf, Rin)  
plt.figure()  
plt.plot(t, Vout_inv, label='Inverting')  
plt.title('Inverting Amplifier')  
plt.grid('true')  
plt.legend()  
plt.show()
```




2. Non-Inverting Amplifier

$$V_o = (1 + R_f/R_1) * V_i$$


```
In [6]: def non_inverting_amplifier(Vin, Rf, R1):
        Av = 1 + (Rf / R1)
        return Av * Vin

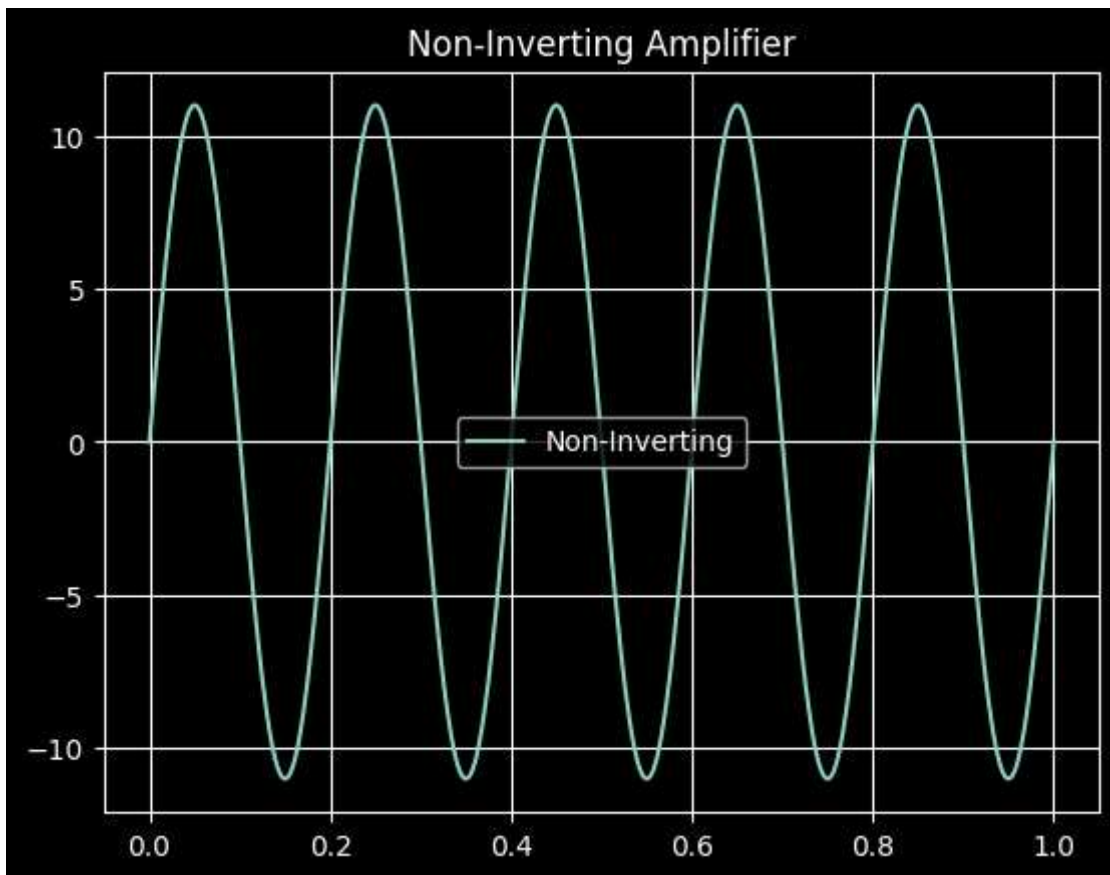Vout_noninv = non_inverting_amplifier(Vin, Rf, R1)
plt.figure()
plt.plot(t, Vout_noninv, label='Non-Inverting')
plt.title('Non-Inverting Amplifier')
plt.grid('true')
plt.legend()
plt.show()
```



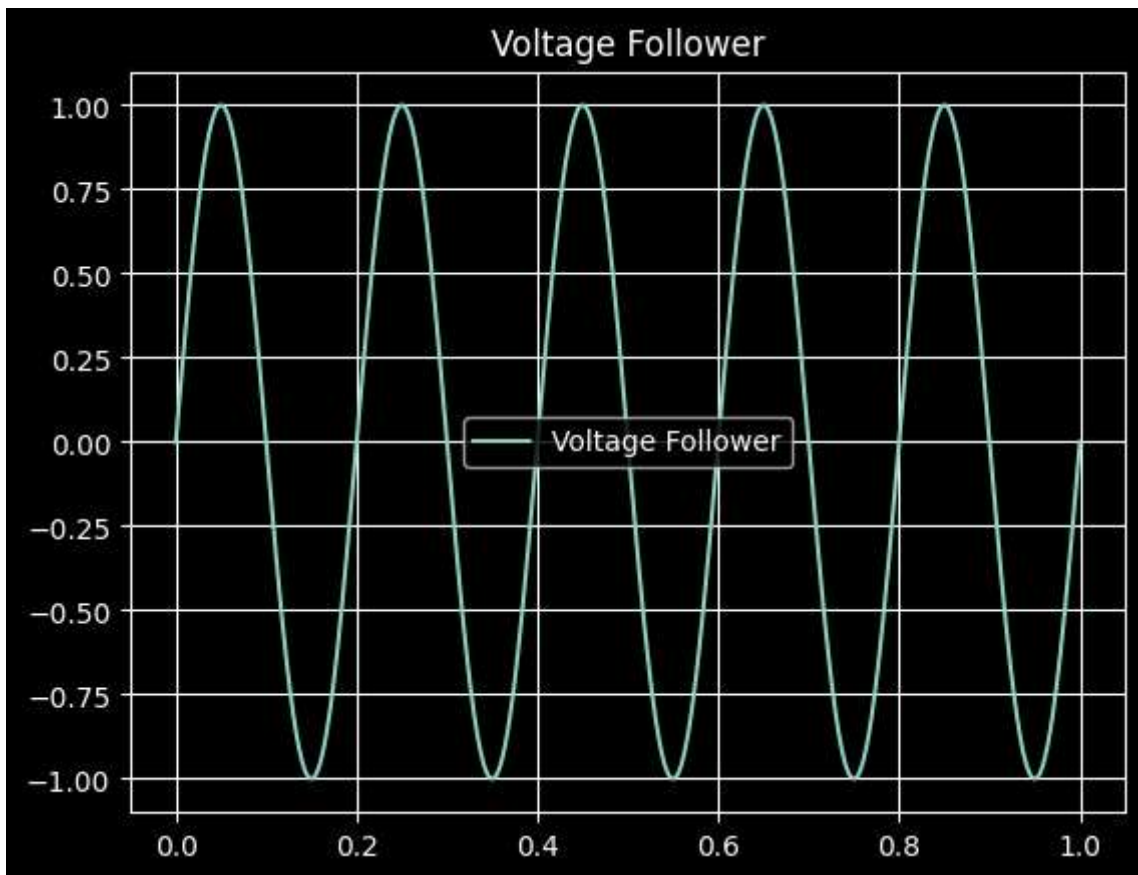3. Voltage Follower (Buffer)

```
In [7]: def voltage_follower(Vin):  
        return Vin  
  
Vout_follow = voltage_follower(Vin)  
plt.figure()  
plt.plot(t, Vout_follow, label='Voltage Follower')  
plt.title('Voltage Follower')  
plt.grid('true')  
plt.legend()  
plt.show()
```




4. Summing Amplifier

$$V_{out} = -((R_f/R_1) * V_{in1} + (R_f/R_2) * V_{in2})$$

```
In [9]: def summing_amplifier(Vin1, Vin2, Rf, R1, R2):
        return -((Rf/R1) * Vin1 + (Rf/R2) * Vin2)

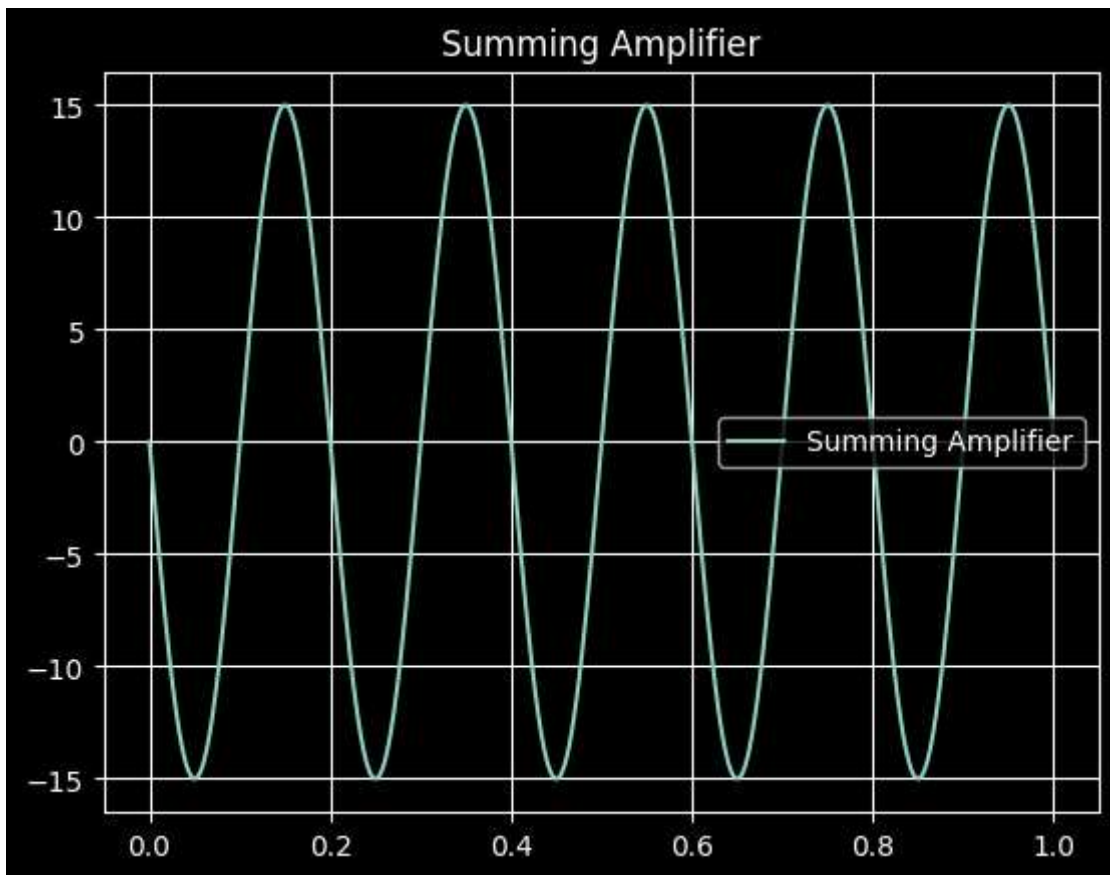Vout_sum = summing_amplifier(Vin, Vin / 2, Rf, R1, R2)
plt.figure()
plt.plot(t, Vout_sum, label='Summing Amplifier')
plt.title('Summing Amplifier')
plt.grid('true')
plt.legend()
plt.show()
```




5. Integrator

$$V_{out} = -(1/(R * C)) * \text{integral}(V_{in})$$

```
In [11]: def integrator(Vin, R, C, t):
          return (-1 / (R * C)) * np.cumsum(Vin) * (t[1] - t[0])

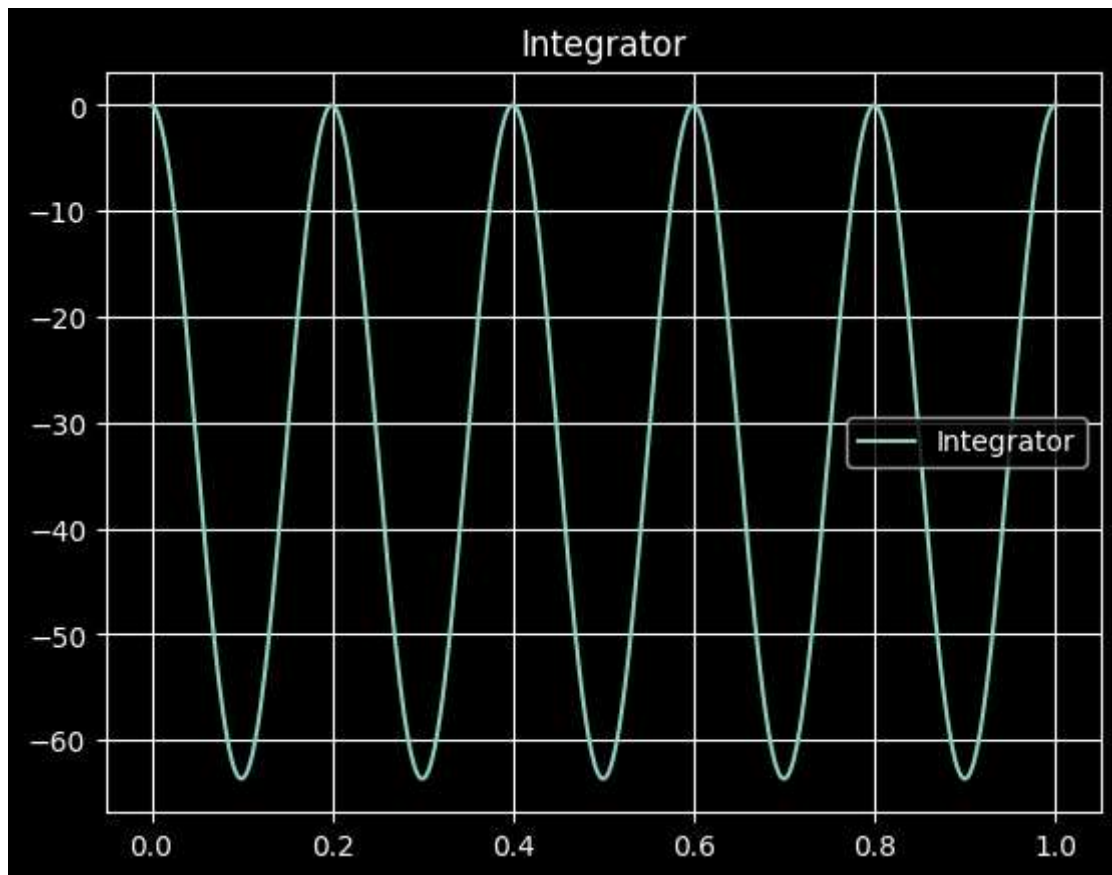Vout_int = integrator(Vin, R1, C, t)
plt.figure()
plt.plot(t, Vout_int, label='Integrator')
plt.title('Integrator')
plt.grid('true')
plt.legend()
plt.show()
```




6. Differentiator

$$V_{out} = -R * C * d(V_{in})/dt$$


```
In [10]: def differentiator(Vin, R, C, t):
          return -R * C * np.gradient(Vin, t)

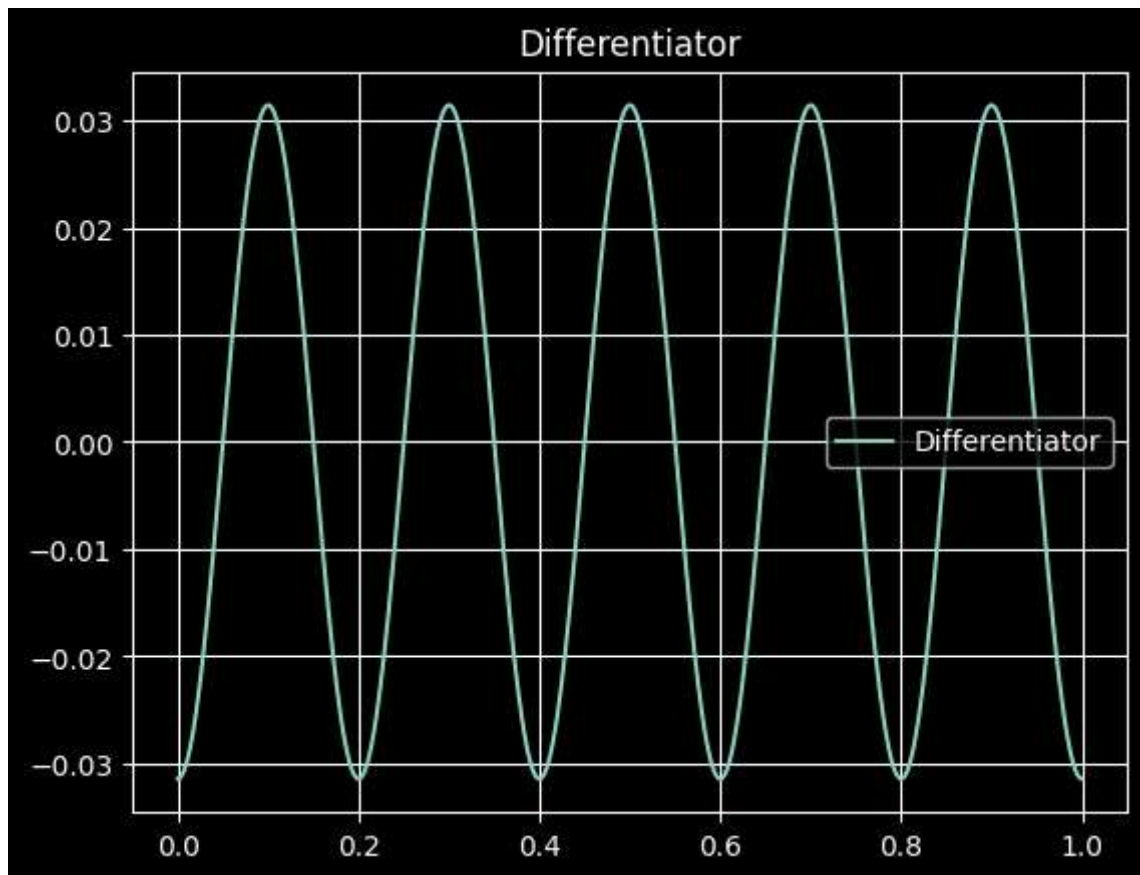Vout_diff = differentiator(Vin, R1, C, t)
plt.figure()
plt.plot(t, Vout_diff, label='Differentiator')
plt.title('Differentiator')
plt.grid('true')
plt.legend()
plt.show()
```



7. Active Low Pass Filter


```
In [12]: def low_pass_filter(Vin, R, C, t):  
    tau = R * C  
    return signal.lfilter([1], [tau, 1], Vin)  
  
Vout_lp = low_pass_filter(Vin, R1, C, t)  
plt.figure()  
plt.plot(t, Vout_lp, label='Low Pass Filter')  
plt.title('Active Low Pass Filter')  
plt.grid('true')  
plt.legend()  
plt.show()
```

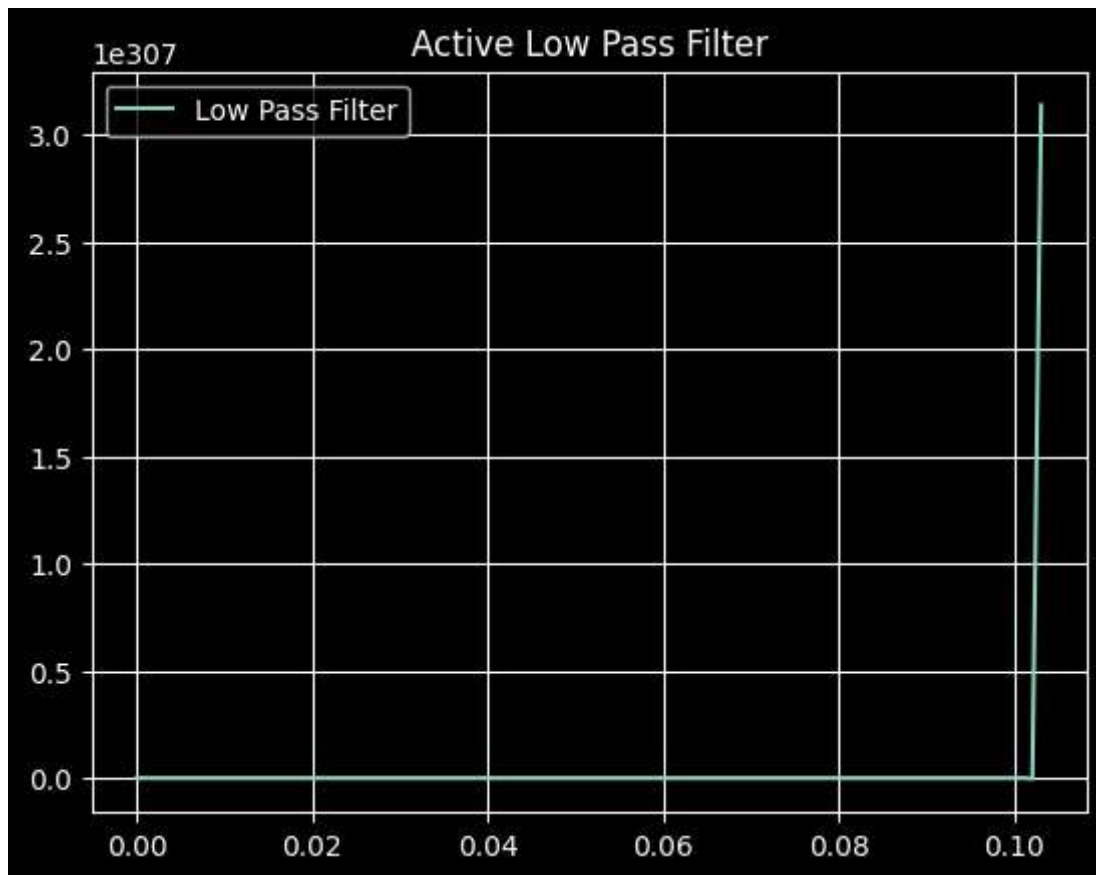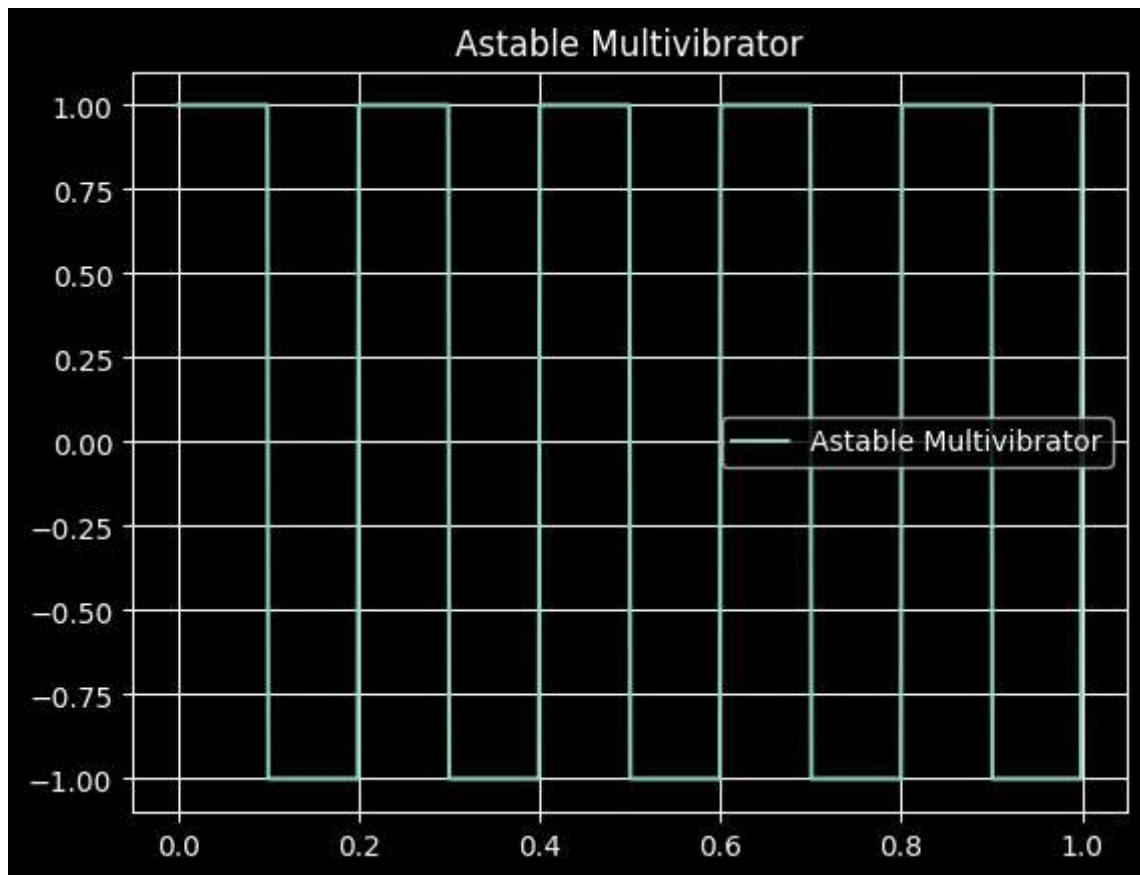8. Astable Multivibrator

```
In [15]: def astable_multivibrator(t, f=5, duty=0.5):
          return signal.square(2 * np.pi * f * t, duty)

Vout_astable = astable_multivibrator(t)
plt.figure()
plt.plot(t, Vout_astable, label='Astable Multivibrator')
plt.title('Astable Multivibrator')
plt.grid('true')
plt.legend()
plt.show()
```



9. Monostable Multivibrator

```
In [16]: def monostable_multivibrator(t, trigger_time=0.2, pulse_duration=0.3):
    Vout_mono = np.zeros_like(t)
    Vout_mono[(t >= trigger_time) & (t <= (trigger_time + pulse_duration))] = 1
    return Vout_mono

Vout_monostable = monostable_multivibrator(t)
plt.figure()
plt.plot(t, Vout_monostable, label='Monostable Multivibrator')
plt.title('Monostable Multivibrator')
plt.grid('true')
plt.legend()
plt.show()
```

